

Informe Pràctica 4-5 - Sistemes Digitals

Sintetitzador de so controlat per CPU

ALEIX GIL & TONI SBERT

June 7, 2016

Continguts

1	Tasca final	2
1.1	Botò	2
1.2	Sintetitzador	2
1.3	Codi final miniAVR i RAM de la cançó	3
1.4	Test Bench simulació	11
1.5	Captures Quartus i simulacions gtkwave	20
1.6	Conclusions	20

1 Tasca final

Implementeu el sintetitzador i dissenyeu un sistema que mentre prems un polsador soni una nota. Feu un disseny en l'entorn Quartus II i carregueu-lo a la tarja DE0-Nano complementada amb la placa adicional d'expansió. Porteu els quatre senyals a la vostra protoboard i munteu el circuit sumador.

1.1 Botò

```
library ieee;
use ieee.std_logic_1164.all;
use ieee.numeric_std.all;

entity botons is
    port (clk,boto: in std_logic;
          flag: out std_logic);
end botons;

architecture behav of botons is
    signal q1,q2: std_logic:='0';

begin
    process(clk)
    begin
        if rising_edge(clk) then
            q1<= boto;
            q2<= q1;
        end if;
    end process;

end behav;
```

1.2 Sintetitzador

Podem veure al codi, com hem implementat un rang de notes, però no les farem servir tots per no allargar massa la cançó i la ROM.

El que fem és demanar un codi midi en binari, que correspon a la nota X i a la seva freqüència corresponent, i extreiem aquesta.

```
library ieee;
use ieee.std_logic_1164.all;
use ieee.numeric_std.all;

entity sintetitzador is
port( midi : in std_logic_vector(7 downto 0);
      clk : in std_logic := '0';
      clock_out : out std_logic);

end sintetitzador;
```

```

architecture behav of sintetitzador is
    signal limit : std_logic_vector(14 downto 0) := "0000000000000000";
    signal count : unsigned(14 downto 0) := (others => '0');
    signal clk_aux : std_logic := '0';
    begin
        with midi select
            limit <=
                "001011001011111" when "00101001", -- Fa 1
                "001001111101110" when "00101011", -- Sol 1

                "000111011101110" when "00110000", -- Do 2
                "000110101001101" when "00110010", -- Re 2
                "000101100101111" when "00110101", -- Fa 2
                "000100111110111" when "00110111", -- Sol 2
                "000100011100001" when "00111001", -- La 2
                "000011111101001" when "00111011", -- Si 2

                "000011101110111" when "00111100", -- Do 3
                "000011010100111" when "00111110", -- Re 3
                "000010111101101" when "01000000", -- Mi 3
                "000010110011000" when "01000001", -- Fa 3
                "000010101001010" when "01001011", -- FA# 3
                "000010011111100" when "01000011", -- Sol 3
                "000010010110110" when "01001100", -- Sol# 3
                "000010001110000" when "01000101", -- La 3
                "000001111110100" when "01000111", -- Si 3

                "000001110111100" when "01001000", -- Do 4
                "000001101010011" when "01001010", -- Re 4

                "000000000000000" when others;

    process(clk)
    begin
        if rising_edge(clk) then
            if count >= unsigned(limit) then
                clk_aux <= not(clk_aux);
                count <= "0000000000000000" ;
            else
                count <= count + 1;
            end if;
            clock_out <= clk_aux;
        end if;
    end process;

end behav;

```

1.3 Codi final miniAVR i RAM de la cançó

Respecte el codi VHDL, hem hagut de modificar les comandes de la ROM, respecte el codi que vam fer servir al laboratori. Podrem visualitzar al final a les captures, com els registres (excepte el 16), fan els canvis de nota corresponents, i els counters es reinicialitzen quan toca.

```

library ieee;
use ieee.std_logic_1164.all;
use ieee.numeric_std.all;

entity mini_avr_01 is
port (clk : in std_logic;
      reset : in std_logic;
      -- Let's have some registers as outputs :
      r16 : out std_logic_vector(7 downto 0);
      r17 : out std_logic_vector(7 downto 0);
      r18 : out std_logic_vector(7 downto 0);
      r19 : out std_logic_vector(7 downto 0));

end mini_avr_01;

architecture behav of mini_avr_01 is

    constant NOP : std_logic_vector(3 downto 0) := "0000";
    constant LDI : std_logic_vector(3 downto 0) := "1110";
    constant ADC : std_logic_vector(3 downto 0) := "0001";
    constant MOV : std_logic_vector(3 downto 0) := "0010";
    constant RJMP : std_logic_vector(3 downto 0) := "1100";
    constant BREQ : std_logic_vector(3 downto 0) := "1111";
    constant BRNE : std_logic_vector(3 downto 0) := "0011";
    constant ALU_MOV : std_logic_vector(2 downto 0) := "010";
    constant ALU_ADC : std_logic_vector(2 downto 0) := "001";
    constant ALU_EOR : std_logic_vector(2 downto 0) := "000";
    constant ALU_AND : std_logic_vector(2 downto 0) := "011";
    constant ALU_OR : std_logic_vector(2 downto 0) := "100";
    constant BRANCH : std_logic_vector(3 downto 0) := "1111";
    constant ALU_B : std_logic_vector(3 downto 0) := "0010";
    constant ALU_B_AND : std_logic_vector(1 downto 0) := "00";
    constant ALU_B_EOR : std_logic_vector(1 downto 0) := "01";
    constant ALU_B_OR : std_logic_vector(1 downto 0) := "10";
    constant ALU_B_MOV : std_logic_vector(1 downto 0) := "11";
    constant IN_OUT : std_logic_vector(3 downto 0) := "1011";
    constant presc_count_limit : std_logic_vector(15 downto 0) := "0000011111010000";

    signal reg_we : std_logic := '0';
    signal nx_reg : std_logic_vector(7 downto 0) := "00000000";
    signal r_reg : std_logic_vector(3 downto 0) := "0000";
    signal d_reg : std_logic_vector(3 downto 0) := "0000";
    signal alu_in_a : std_logic_vector(7 downto 0) := "00000000";
    signal alu_in_b : std_logic_vector(7 downto 0) := "00000000";
    signal pr_op : std_logic_vector(15 downto 0) := "0000000000000000";
    signal pr_pc : std_logic_vector(7 downto 0) := "00000000";
    signal k : std_logic_vector(7 downto 0) := "00000000";
    signal alu_op : std_logic_vector(2 downto 0) := "000";
    signal alu_out : std_logic_vector(7 downto 0) := "00000000";
    signal debug_carry : std_logic := '0';
    signal debug_zero : std_logic := '0';
    signal add_temp : std_logic_vector(9 downto 0) := "0000000000";
    signal nx_pc : std_logic_vector(7 downto 0) := "00000000";

```

```

signal k_jump : std_logic_vector(7 downto 0) := "00000000";
signal update_z : std_logic := '0';
signal c_r16 : std_logic_vector(3 downto 0) := "0000";
signal c_r17 : std_logic_vector(3 downto 0) := "0001";
signal c_r18 : std_logic_vector(3 downto 0) := "0010";
signal c_r19 : std_logic_vector(3 downto 0) := "0011";
signal c_r20 : std_logic_vector(3 downto 0) := "0100";
signal c_r21 : std_logic_vector(3 downto 0) := "0101";
signal c_r22 : std_logic_vector(3 downto 0) := "0110";
signal port_we : std_logic := '0';
signal in_data : std_logic_vector(7 downto 0) := "00000000";
signal timer_count : std_logic_vector(7 downto 0) := "00000000";
signal presc_count : std_logic_vector(15 downto 0) := "0000000000000000";
signal timer_state : std_logic_vector(7 downto 0) := "00000000";
signal port_adr : std_logic_vector(3 downto 0) := "0000";
signal presc_tc : std_logic := '0';
signal port_A8i : std_logic_vector(7 downto 0) := "00000000";
signal port_A9i : std_logic_vector(7 downto 0) := "00000000";
signal timer_limit : std_logic_vector(7 downto 0) := "00000000";

type register_bank is
    array (15 downto 0) of std_logic_vector(7 downto 0);
    signal regs : register_bank; -- Registers r16..r31

type out_mux_type is (mux_alu, mux_lit, mux_in_out);
signal out_mux : out_mux_type;

type status_reg is
    record
        Z : std_logic;
        C : std_logic;
    end record;
signal pr_SR, nx_SR : status_reg;

begin

RegW : process(clk) -- Register write
begin
    if rising_edge(clk) then
        if reg_we = '1' then -- write
            regs(to_integer(unsigned(d_reg))) <= nx_reg;
        end if;
    end if;
end process RegW;

-- Register read : ALU inputs
alu_in_a <= regs(to_integer(unsigned(d_reg)));
alu_in_b <= regs(to_integer(unsigned(r_reg)));

ROM : process(pr_pc) -- Program ROM
begin
    case pr_pc is
        -- LA(2) => pr_op <= LDI & "0011" & c_r16 & "1001";
    end case;
end process ROM;

```

```

-- SI(2) => pr_op <= LDI & "0011" & c_r16 & "1011";
-- DO(3) => pr_op <= LDI & "0011" & c_r16 & "1100";
-- RE(3) => pr_op <= LDI & "0011" & c_r16 & "1110";
-- MI(3) => pr_op <= LDI & "0100" & c_r16 & "0000";
-- FA#(3) => pr_op <= LDI & "0100" & c_r16 & "1011";

when X"00" => pr_op <= LDI & "0011" & c_r16 & "1001"; -- LA 2
when X"01" => pr_op <= LDI & "0011" & c_r17 & "1001"; -- LA 2
when X"02" => pr_op <= LDI & "0011" & c_r18 & "1001"; -- LA 2
when X"03" => pr_op <= LDI & "0011" & c_r19 & "1001"; -- LA 2

when X"04" => pr_op <= LDI & "0000" & c_r20 & "0000";
when X"05" => pr_op <= LDI & "1010" & c_r22 & "1010"; --carga el 170 en el 22
when X"06" => pr_op <= IN_OUT & "1000" & c_r22 & "1010"; --out registres
when X"07" => pr_op <= IN_OUT & "0000" & c_r21 & "0010";
when X"08" => pr_op <= ALU_B & ALU_B_OR & "11" & c_r21 & c_r20; --Or dels registres 21 i 20
when X"09" => pr_op <= BREQ & "00" & "0000001" & "101"; -- Si no es igual bota 2 posicions i
when X"0A" => pr_op <= RJMP & "----" & "1111" & "1100"; --Salta -3

when X"0B" => pr_op <= LDI & "0011" & c_r16 & "1100"; -- DO 3
when X"0C" => pr_op <= LDI & "0011" & c_r17 & "1100"; -- DO 3
when X"0D" => pr_op <= LDI & "0011" & c_r18 & "1100"; -- DO 3
when X"0E" => pr_op <= LDI & "0011" & c_r19 & "1100"; -- DO 3

when X"0F" => pr_op <= LDI & "0000" & c_r20 & "0000";
when X"10" => pr_op <= LDI & "1010" & c_r22 & "1010"; --carga el 170 en el 22
when X"11" => pr_op <= IN_OUT & "1000" & c_r22 & "1010"; --out registres
when X"12" => pr_op <= IN_OUT & "0000" & c_r21 & "0010";
when X"13" => pr_op <= ALU_B & ALU_B_OR & "11" & c_r21 & c_r20; --Or dels registres 21 i 20
when X"14" => pr_op <= BREQ & "00" & "0000001" & "101"; -- Si no es igual bota 2 posicions i
when X"15" => pr_op <= RJMP & "----" & "1111" & "1100"; --Sa

when X"16" => pr_op <= LDI & "0011" & c_r16 & "1110"; -- RE 3
when X"17" => pr_op <= LDI & "0011" & c_r17 & "1110"; -- RE 3
when X"18" => pr_op <= LDI & "0011" & c_r18 & "1110"; -- RE 3
when X"19" => pr_op <= LDI & "0011" & c_r19 & "1110"; -- RE 3

when X"1A" => pr_op <= LDI & "0000" & c_r20 & "0000";
when X"1B" => pr_op <= LDI & "1010" & c_r22 & "1010"; --carga el 170 en el 22
when X"1C" => pr_op <= IN_OUT & "1000" & c_r22 & "1010"; --out registres
when X"1D" => pr_op <= IN_OUT & "0000" & c_r21 & "0010";
when X"1E" => pr_op <= ALU_B & ALU_B_OR & "11" & c_r21 & c_r20; --Or dels registres 21 i 20
when X"1F" => pr_op <= BREQ & "00" & "0000001" & "101"; -- Si no es igual bota 2 posicions i
when X"20" => pr_op <= RJMP & "----" & "1111" & "1100"; --Sa

when X"21" => pr_op <= LDI & "0100" & c_r16 & "1011"; -- FA# 3
when X"22" => pr_op <= LDI & "0100" & c_r17 & "1011"; -- FA# 3
when X"23" => pr_op <= LDI & "0100" & c_r18 & "1011"; -- FA# 3
when X"24" => pr_op <= LDI & "0100" & c_r19 & "1011"; -- FA# 3

when X"25" => pr_op <= LDI & "0000" & c_r20 & "0000";
when X"26" => pr_op <= LDI & "1010" & c_r22 & "1010"; --carga el 170 en el 22
when X"27" => pr_op <= IN_OUT & "1000" & c_r22 & "1010"; --out registres
when X"28" => pr_op <= IN_OUT & "0000" & c_r21 & "0010";

```

```

when X"29" => pr_op <= ALU_B & ALU_B_OR & "11" & c_r21 & c_r20;--Or dels registres 21 i 20
when X"2A" => pr_op <= BREQ & "00" & "0000001" & "101";-- Si no es igual bota 2 posicions i
when X"2B" => pr_op <= RJMP & "----" & "1111" & "1100";--Sa

when X"2C" => pr_op <= LDI & "0011" & c_r16 & "1001"; -- LA 2
when X"2D" => pr_op <= LDI & "0011" & c_r17 & "1001"; -- LA 2
when X"2E" => pr_op <= LDI & "0011" & c_r18 & "1001"; -- LA 2
when X"2F" => pr_op <= LDI & "0011" & c_r19 & "1001"; -- LA 2

when X"30" => pr_op <= LDI & "0000" & c_r20 & "0000";
when X"31" => pr_op <= LDI & "1010" & c_r22 & "1010";--carga el 170 en el 22
when X"32" => pr_op <= IN_OUT & "1000" & c_r22 & "1010";--out registres
when X"33" => pr_op <= IN_OUT & "0000" & c_r21 & "0010";
when X"34" => pr_op <= ALU_B & ALU_B_OR & "11" & c_r21 & c_r20;--Or dels registres 21 i 20
when X"35" => pr_op <= BREQ & "00" & "0000001" & "101";-- Si no es igual bota 2 posicions i
when X"36" => pr_op <= RJMP & "----" & "1111" & "1100";--Sa

when X"37" => pr_op <= LDI & "0011" & c_r16 & "1011"; -- SI 2
when X"38" => pr_op <= LDI & "0011" & c_r17 & "1011"; -- SI 2
when X"39" => pr_op <= LDI & "0011" & c_r18 & "1011"; -- SI 2
when X"3A" => pr_op <= LDI & "0011" & c_r19 & "1011"; -- SI 2

when X"3B" => pr_op <= LDI & "0000" & c_r20 & "0000";
when X"3C" => pr_op <= LDI & "1010" & c_r22 & "1010";--carga el 170 en el 22
when X"3D" => pr_op <= IN_OUT & "1000" & c_r22 & "1010";--out registres
when X"3E" => pr_op <= IN_OUT & "0000" & c_r21 & "0010";
when X"3F" => pr_op <= ALU_B & ALU_B_OR & "11" & c_r21 & c_r20;--Or dels registres 21 i 20
when X"40" => pr_op <= BREQ & "00" & "0000001" & "101";-- Si no es igual bota 2 posicions i
when X"41" => pr_op <= RJMP & "----" & "1111" & "1100";--Sa

when X"42" => pr_op <= LDI & "0011" & c_r16 & "1110"; -- RE 3
when X"43" => pr_op <= LDI & "0011" & c_r17 & "1110"; -- RE 3
when X"44" => pr_op <= LDI & "0011" & c_r18 & "1110"; -- RE 3
when X"45" => pr_op <= LDI & "0011" & c_r19 & "1110"; -- RE 3

when X"46" => pr_op <= LDI & "0000" & c_r20 & "0000";
when X"47" => pr_op <= LDI & "1010" & c_r22 & "1010";--carga el 170 en el 22
when X"48" => pr_op <= IN_OUT & "1000" & c_r22 & "1010";--out registres
when X"49" => pr_op <= IN_OUT & "0000" & c_r21 & "0010";
when X"4A" => pr_op <= ALU_B & ALU_B_OR & "11" & c_r21 & c_r20;--Or dels registres 21 i 20
when X"4B" => pr_op <= BREQ & "00" & "0000001" & "101";-- Si no es igual bota 2 posicions i
when X"4C" => pr_op <= RJMP & "----" & "1111" & "1100";--Sa

when X"4D" => pr_op <= LDI & "0100" & c_r16 & "0000"; -- MI 3
when X"4E" => pr_op <= LDI & "0100" & c_r17 & "0000"; -- MI 3
when X"4F" => pr_op <= LDI & "0100" & c_r18 & "0000"; -- MI 3
when X"50" => pr_op <= LDI & "0100" & c_r19 & "0000"; -- MI 3

when others => pr_op <= ( others => '-' );
end case;

end process;

```



```

CONTROL : process(pr_op,pr_pc,pr_SR)
begin
    r_reg <= (others => '-'); -- Defaults
    d_reg <= (others => '-');
    k <= (others => '-');
    ALU_op <= (others => '-');
    reg_we <= '0';
    k_jump <= (others => '0');
    port_we <= '0';
    case pr_op(15 downto 12) is -- These bits are enough to
-- decide among our reduced
-- instruction set!

        when LDI => ----- LDI Instruction
            d_reg <= pr_op(7 downto 4);
            out_mux <= mux_lit ;
            k <= pr_op(11 downto 8) & pr_op(3 downto 0);
            reg_we <= '1';

        when ADC => ----- ADC Instruction
            r_reg <= pr_op(3 downto 0);
            d_reg <= pr_op(7 downto 4);
            out_mux <= mux_alu;
            reg_we <= '1';
-- Enable register write
            ALU_op <= ALU_ADC;

        when ALU_B => ----- MOV,AND,EOR,OR Instructions
            reg_we <= '1'; -- Enable register write
            case pr_op(11 downto 10) is -- Decode further down
                when ALU_B_MOV => ALU_op <= ALU_MOV;
                when ALU_B_EOR => ALU_op <= ALU_EOR;
                when ALU_B_AND => ALU_op <= ALU_AND;
                when ALU_B_OR => ALU_op <= ALU_OR;
                when others => null;
            end case;

        when BRANCH => ----- BRANCH Instruction
            if pr_op(10) = '0' then -- BREQ Instruction
                if pr_SR.Z = '1' then
                    k_jump(6 downto 0) <= pr_op(9 downto 3);
                    k_jump(7) <= pr_op(9);
                end if;
            else
                if pr_SR.Z = '0' then -- Si el Z no està actiu
                    k_jump(6 downto 0) <= pr_op(9 downto 3); -- Posa k_jump al valor indicat per l'OPCODE
                    k_jump(7) <= pr_op(9);
                end if;
            end if;
    end case;
end process;

```

```

when RJMP =>
    k_jump<= pr_op(7 downto 0);

when IN_OUT =>
    if pr_op(11) = '1' then -- OUT
        port_we <= '1';
        port_adr <= pr_op(3 downto 0);
        r_reg <= pr_op(7 downto 4);
    else -- IN
        out_mux <= mux_in_out;
        d_reg <= pr_op (7 downto 4); -- Destination register
        reg_we <= '1';
        case pr_op (1 downto 0) is -- Decode IN address
            when "10" => in_data <= timer_state;
            when others => null;
        end case;
    end if;

when others =>
    null;
end case;
end process;

ALU : process(alu_op,alu_in_a,alu_in_b,pr_SR,add_temp)
begin
    nx_SR.C <= pr_SR.C; -- by default, preserve status register
    update_Z <= '1';
    case alu_op is
        when ALU_MOV =>
            alu_out <= alu_in_b;
            update_Z <= '0';
        when ALU_AND =>
            alu_out <= alu_in_a and alu_in_b;
        when ALU_OR =>
            alu_out <= alu_in_a or alu_in_b;
        when ALU_EOR =>
            alu_out <= alu_in_a xor alu_in_b;
        when ALU_ADC => ----- ADC : Carry in / out
            add_temp <= std_logic_vector( -- auxiliar SLV (9..0)
                unsigned('0' & alu_in_a & '1') + unsigned('0' & alu_in_b & pr_SR.C )); -- Carry In
            alu_out <= add_temp(8 downto 1);
            nx_SR.C <= add_temp(9); -- Update Carry Flag

        when others => ----- Should not happen
            alu_out <= (others => '-'); -- Don't care
    end case;
end process;

```

```

end process;

UPD_z : process ( update_Z , alu_out , pr_SR )
begin
    if update_Z = '1' then -- - - - - - Update Zero Flag
        if alu_out = x"00" then
            nx_SR . Z <= '1';
        else
            nx_SR . Z <= '0';
        end if;
    else
        ----- Keep old value
        nx_SR . Z <= pr_SR . Z ;
    end if;
end process;

MUX : process(out_mux, alu_out, k, in_data)
begin
    case out_mux is
        when mux_alu => nx_reg <= alu_out;
        when mux_lit => nx_reg <= k;
        when mux_in_out => nx_reg <= in_data;
        when others => nx_reg <= (others => '-');
    end case;
end process;

process(clk,reset) -- Synchronous elements
begin
    if reset = '1' then -- Initialize Processor
        pr_pc <= ( others => '0');
        pr_SR.C <= '0';
        pr_SR.Z <= '0';
    elsif(rising_edge(clk)) then
        pr_pc <= nx_pc;
        pr_SR <= nx_SR;
    end if;
end process;

--nx_pc <= std_logic_vector(unsigned(pr_pc) + 1);

r16 <= regs(0);
r17 <= regs(1);
r18 <= regs(2);
r19 <= regs(3);
debug_carry <= pr_SR.C;
debug_zero <= pr_SR.Z;

NEXT_PC : process (pr_pc,k_jmp)
    variable tmp_pc : std_logic_vector(8 downto 0);
begin
    tmp_pc := std_logic_vector(signed(pr_pc & '1') + signed(k_jmp & '1'));
    nx_pc <= tmp_pc (8 downto 1);
end process;

```

```

process(clk)
begin
    if rising_edge(clk) then
        if port_we = '1' and port_adr = "1010" then -- reset counter
            timer_count <= (others => '0'); -- when writing
            presc_count <= (others => '0'); -- new timer_limit
        else
            if timer_state /= x"00" and presc_tc = '1' then
                timer_count <=
                    std_logic_vector(unsigned(timer_count)+1);
            end if;
            if presc_tc = '1' then
                presc_count <= (others => '0');
            else
                presc_count <=
                    std_logic_vector(unsigned(presc_count)+1);
            end if;
        end if;
    end if;
end process;

timer_state <= x"00" when timer_count = timer_limit -- 1:counting 0:finished
               else x"01";
presc_tc <= '1' when presc_count = presc_count_limit -- constant
           else '0';

```

```

PortW: process(clk)
begin
    if rising_edge(clk) then
        if port_we = '1' then
            case port_adr is
                when "1000" =>
                    port_A8i <= regs(to_integer(unsigned(r_reg)));
                when "1001" =>
                    port_A9i <= regs(to_integer(unsigned(r_reg)));
                when "1010" =>
                    timer_limit <= regs(to_integer(unsigned(r_reg)));
                when others => null;
            end case;
        end if;
    end if;
end process PortW;

```

```
end behav;
```

1.4 Test Bench simulació

Hem fet aquesta quantitat de temps per poder veure que la durada de les notes era la correcta i era perceptible pel oïda humana.

```
library ieee;
use ieee.std_logic_1164.all;
use ieee.numeric_std.all;

entity mini_avr_01_tb is
end mini_avr_01_tb;

architecture behav of mini_avr_01_tb is
    component my_mini_avr_01
        port( clk, reset : in std_logic;
              r16, r17, r18, r19 : out std_logic_vector(7 downto 0));
    end component;
    for dut : my_mini_avr_01 use entity work.mini_avr_01;

    signal clk, reset : std_logic;
    signal r16, r17, r18, r19 : std_logic_vector(7 downto 0);

begin

    dut : my_mini_avr_01 port map ( clk => clk,
                                    reset => reset,
                                    r16 => r16,
                                    r17 => r17,
                                    r18 => r18,
                                    r19 => r19);

    clk0_process: process
    begin
        -- inicialitzar la cpu, flanc de reset

        clk <= '0';
        reset <= '1';
        wait for 500 ns;
        clk <= '1';
        wait for 500 ns;
        reset <= '0';
        for i in 1 to 200000 loop
            clk <= not clk;
            wait for 500 ns;
        end loop;
        for i in 1 to 200000 loop
            clk <= not clk;
            wait for 500 ns;
        end loop;
        for i in 1 to 200000 loop
            clk <= not clk;
            wait for 500 ns;
        end loop;
        for i in 1 to 200000 loop
            clk <= not clk;
            wait for 500 ns;
        end loop;
        for i in 1 to 200000 loop
            clk <= not clk;
        end loop;
    end process;
end;
```

```
wait for 500 ns;
end loop;
    for i in 1 to 200000 loop
clk <= not clk;
wait for 500 ns;
end loop;
        for i in 1 to 200000 loop
clk <= not clk;
wait for 500 ns;
end loop;
for i in 1 to 200000 loop
clk <= not clk;
wait for 500 ns;
end loop;
for i in 1 to 200000 loop
clk <= not clk;
wait for 500 ns;
end loop;
    for i in 1 to 200000 loop
clk <= not clk;
wait for 500 ns;
end loop;
        for i in 1 to 200000 loop
clk <= not clk;
wait for 500 ns;
end loop;
            for i in 1 to 200000 loop
clk <= not clk;
wait for 500 ns;
end loop;
                for i in 1 to 200000 loop
clk <= not clk;
wait for 500 ns;
end loop;
                    for i in 1 to 200000 loop
clk <= not clk;
wait for 500 ns;
end loop;
                        for i in 1 to 200000 loop
clk <= not clk;
wait for 500 ns;
end loop;
                            for i in 1 to 200000 loop
clk <= not clk;
wait for 500 ns;
end loop;
                                for i in 1 to 200000 loop
clk <= not clk;
wait for 500 ns;
end loop;
```

```

        for i in 1 to 200000 loop
            clk <= not clk;
            wait for 500 ns;
        end loop;
        for i in 1 to 200000 loop
            clk <= not clk;
            wait for 500 ns;
        end loop;
        for i in 1 to 200000 loop
            clk <= not clk;
            wait for 500 ns;
        end loop;
        for i in 1 to 200000 loop
            clk <= not clk;
            wait for 500 ns;
        end loop;
        for i in 1 to 200000 loop
            clk <= not clk;
            wait for 500 ns;
        end loop;
        for i in 1 to 200000 loop
            clk <= not clk;
            wait for 500 ns;
        end loop;
        for i in 1 to 200000 loop
            clk <= not clk;
            wait for 500 ns;
        end loop;
        for i in 1 to 200000 loop
            clk <= not clk;
            wait for 500 ns;
        end loop;
        for i in 1 to 200000 loop
            clk <= not clk;
            wait for 500 ns;
        end loop;
        wait;
    end process clk0_process;

process
    begin
        wait;
        -- Enter here your simulation sequence
    end process;
end behav;
```

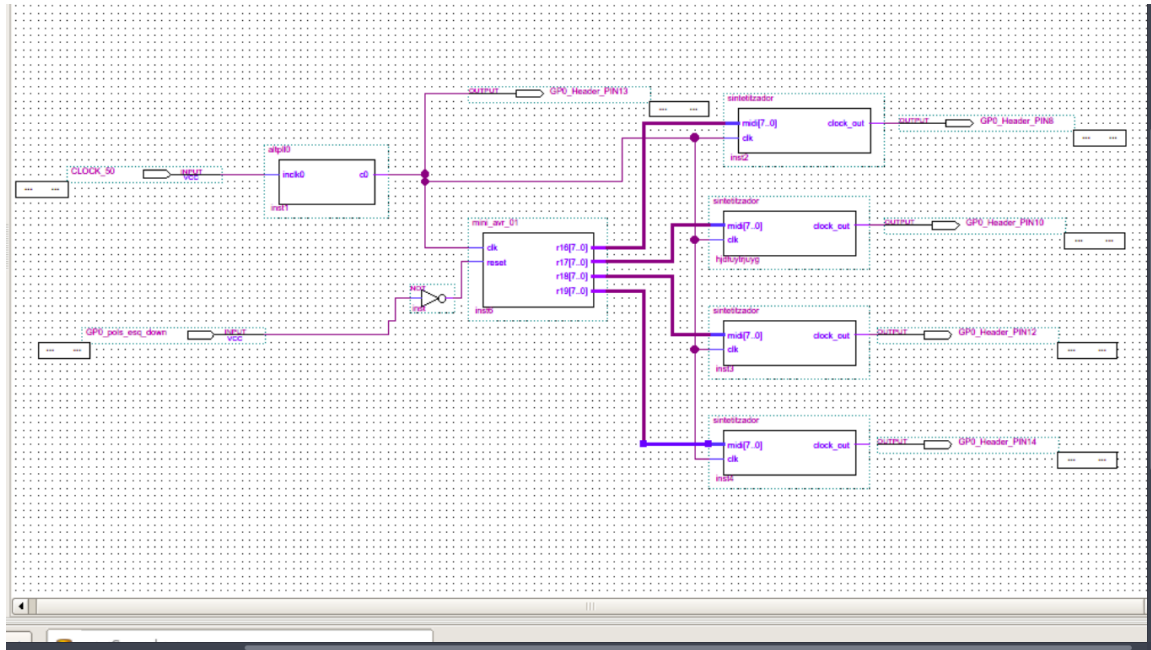


Figure 1: Fotografia Quartus, implementació cançó final (miniAVR)

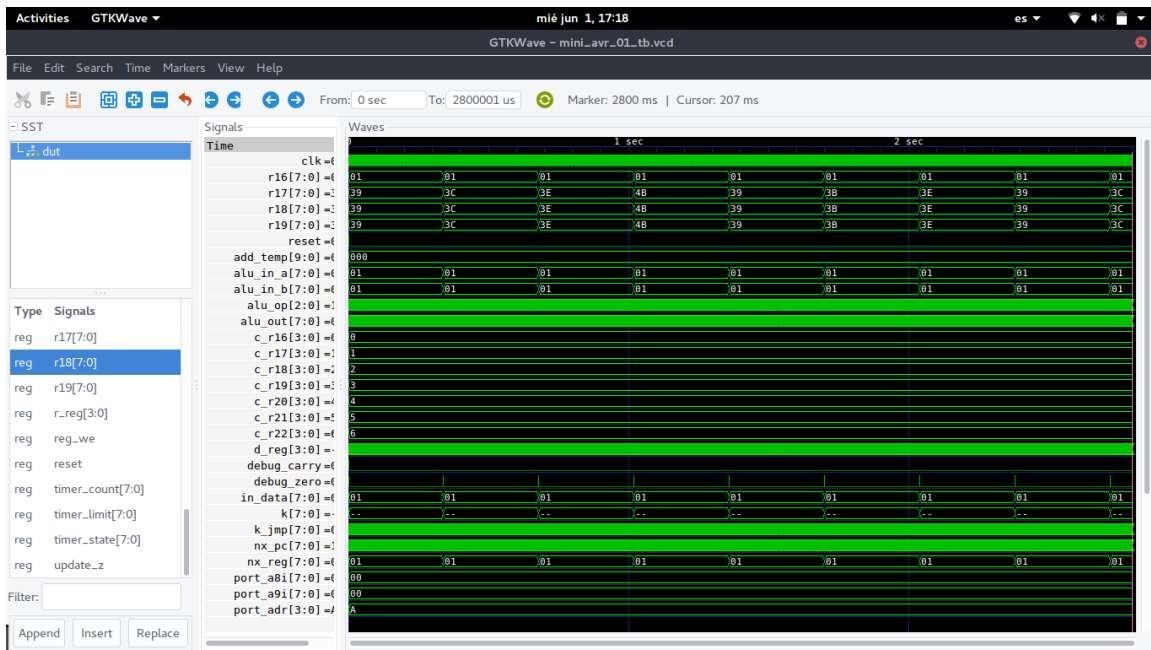


Figure 2: Simulació general (1)

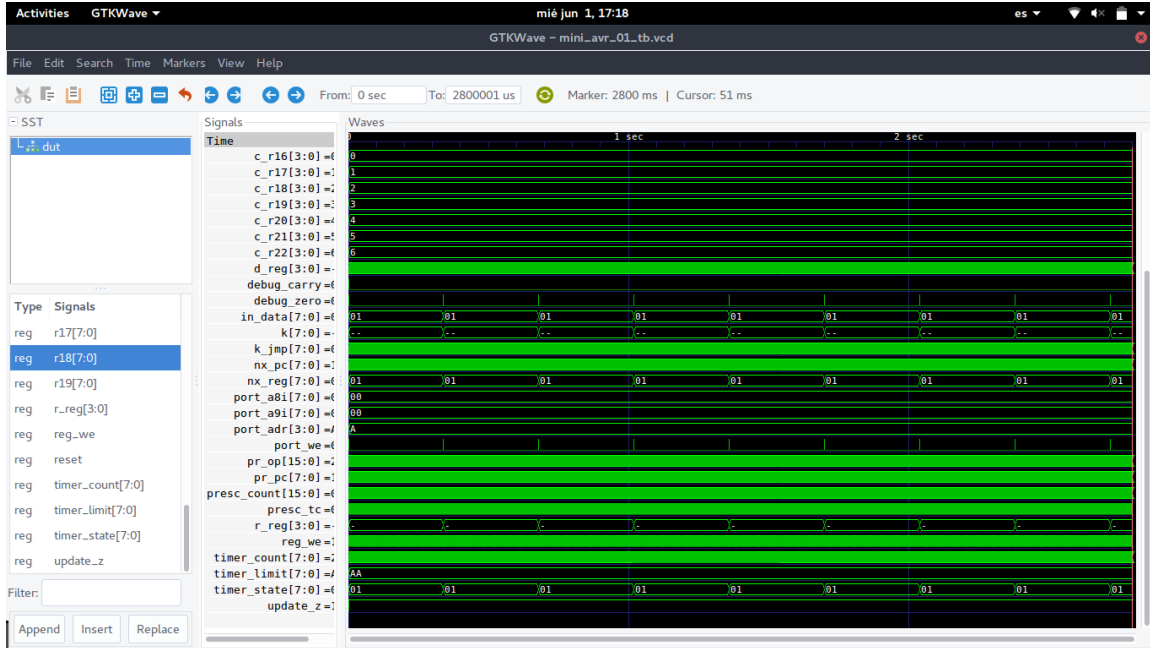


Figure 3: Simulació general (2)

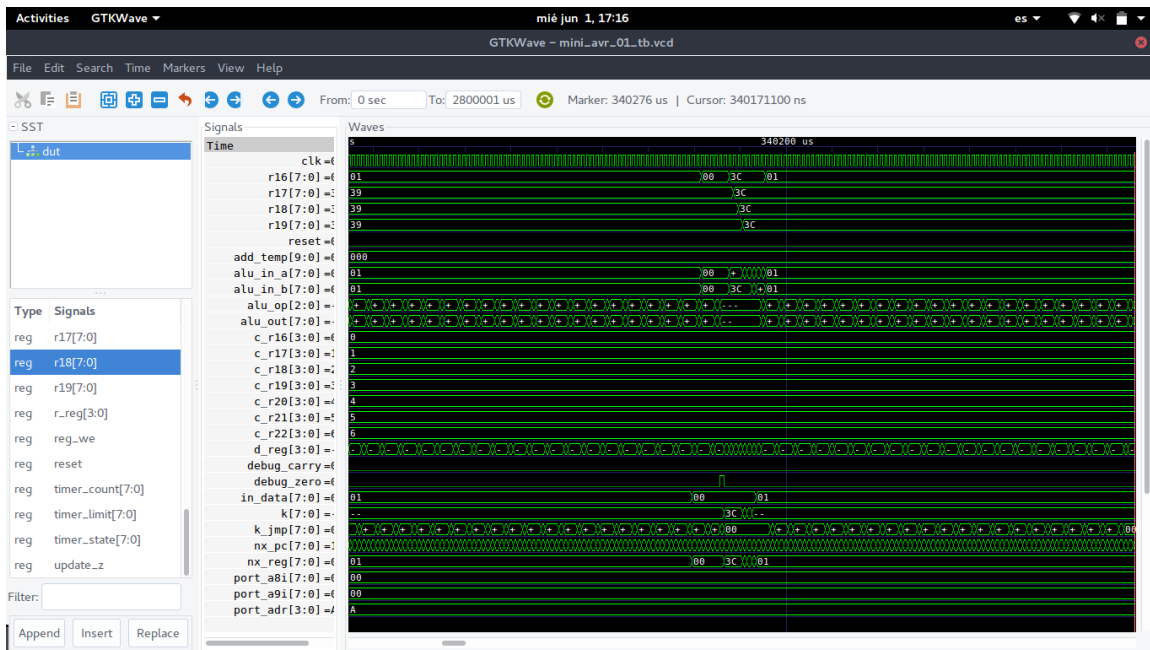


Figure 4: Primer zoom (1)

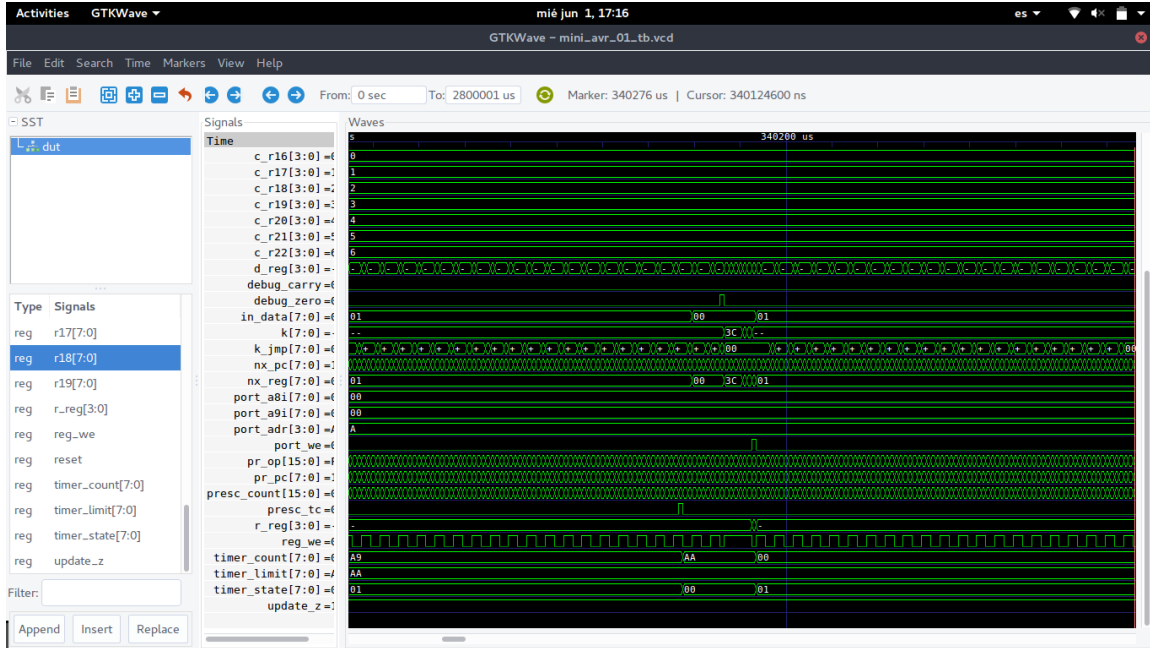


Figure 5: Primer zoom (2)

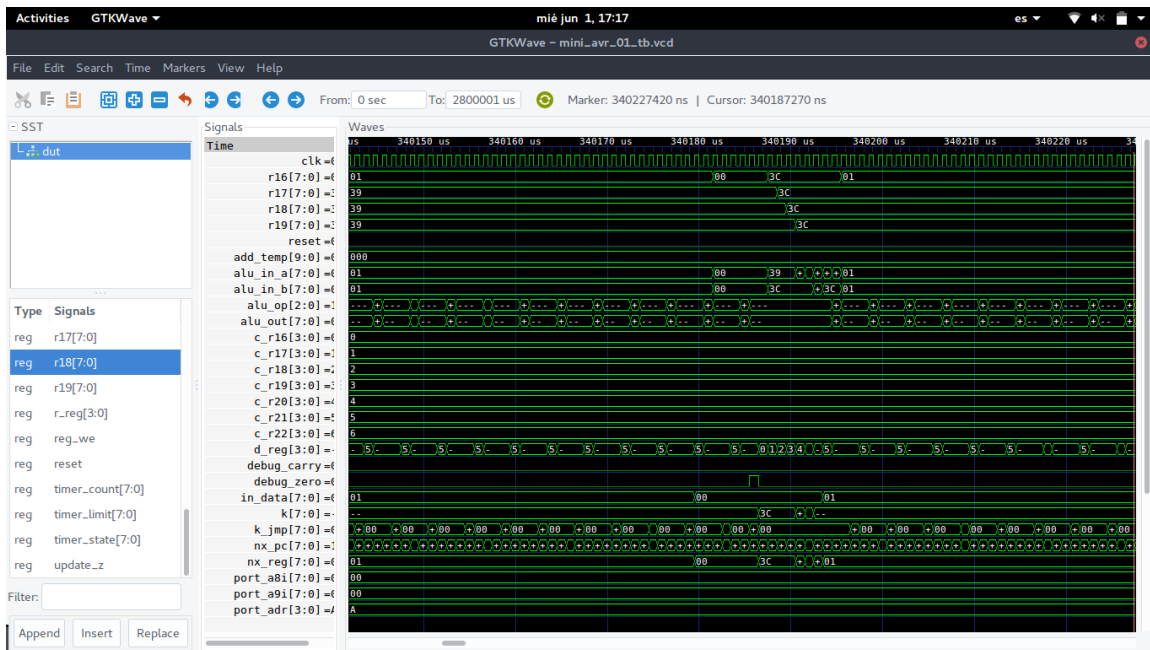


Figure 6: Segon zoom (1)

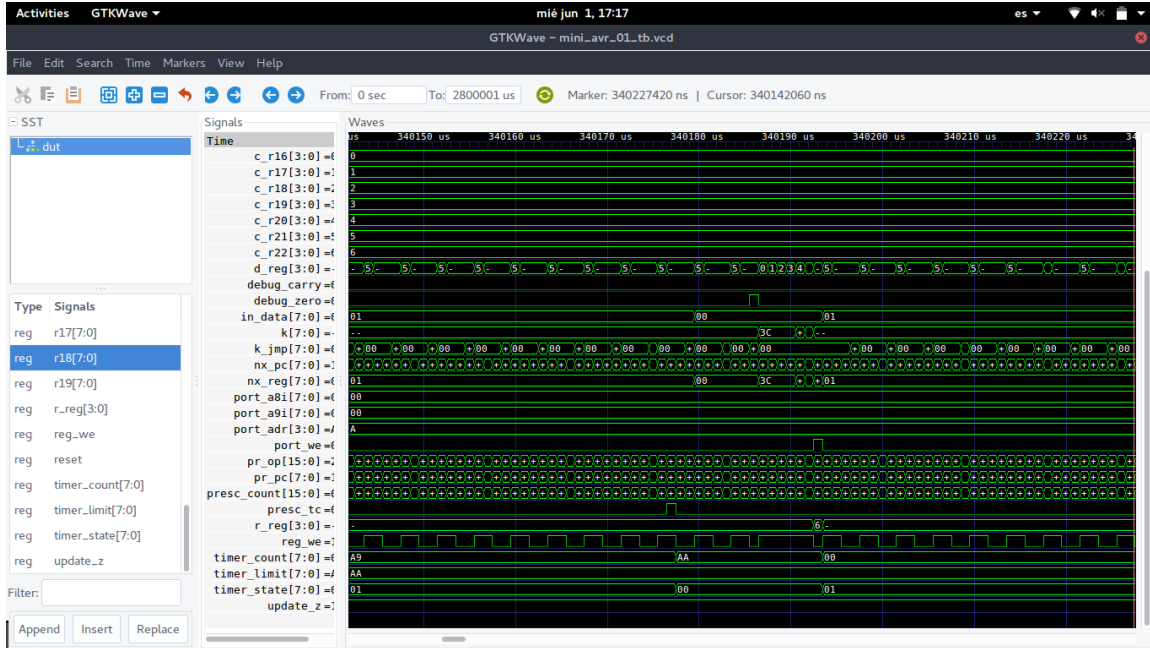


Figure 7: Segon zoom (2)

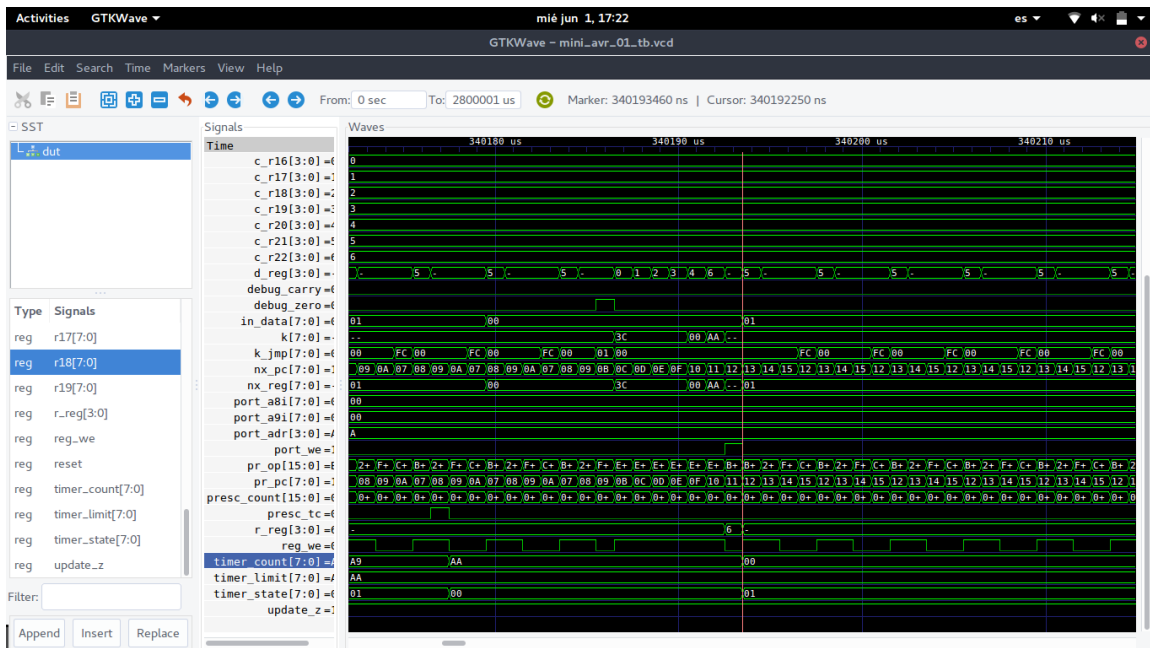


Figure 8: Reinici timer count

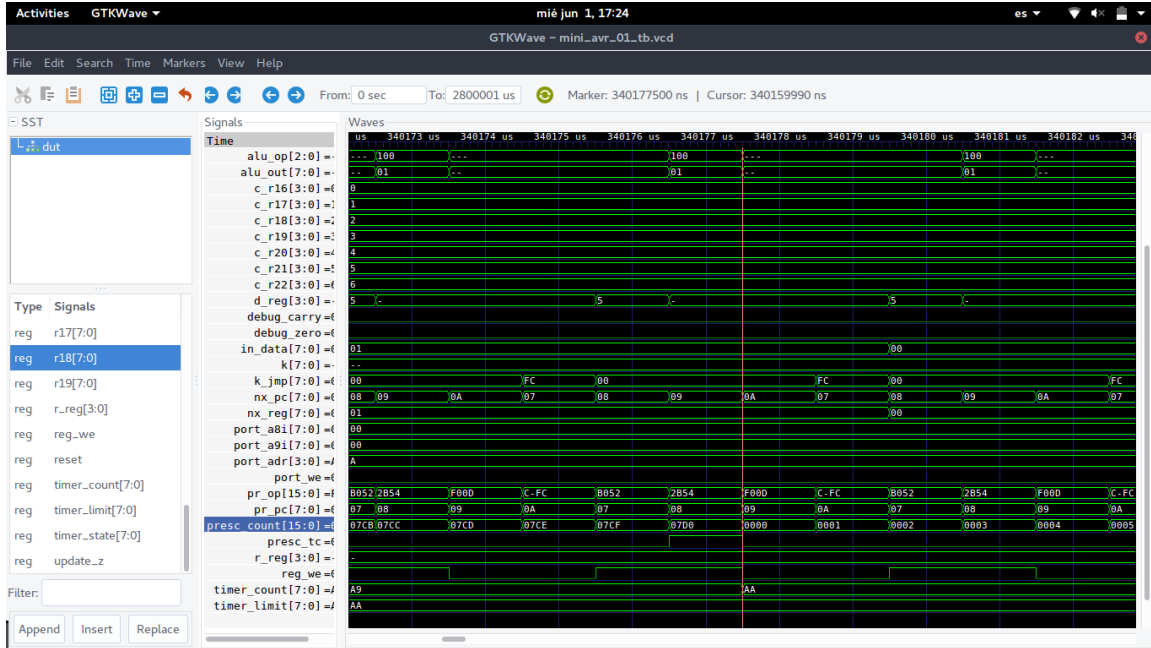


Figure 9: Reinici prescaler count

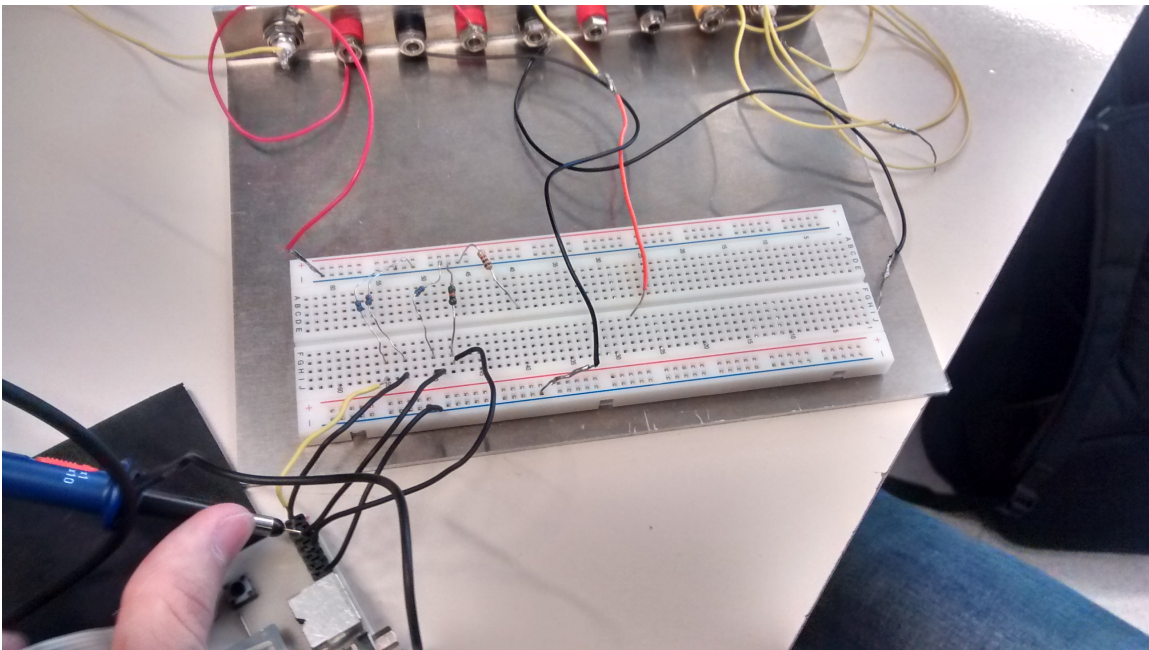


Figure 10: Connexió protoboard

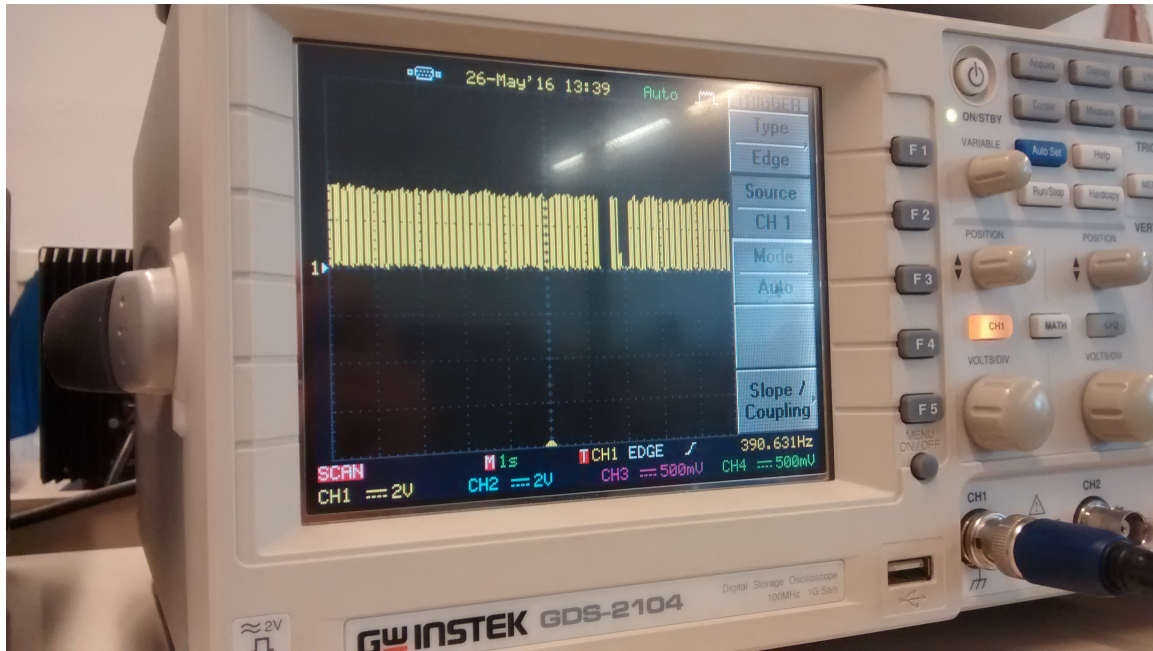


Figure 11: Oscil·loscopi

1.5 Captures Quartus i simulacions gtkwave

1.6 Conclusions

Al laboratori, no ens sonaven les notes com corresponien. Ens produïa canvis quan polsàvem el botó. No sabem el motiu exacte, però degut al codi no creiem que s'hagin produït els errors, pot ésser que els FPGA que vam utilitzar tinguessin algun error ja que, uns companys de classe ens van dir que n'hi havia una amb botons defectuosos i potser per això no ens hagi acabat de funcionar com cal. Però, també podria ser un error del timer ja que, en primera instància amb el codi del previ no feia el RJMP bé però que, durant les pràctiques vam corregir el codi i a les simulacions funciona perfectament.

Ara, però amb les noves simulacions podem veure que funciona correctament.